

# 1EM1: Basic Electrical Measurements

## OBJECTIVES

1. To become familiar with the basic methods of measuring voltage, current, and resistance.
2. To be acquainted with the use of an oscilloscope.

## THEORY

### Digital Storage Oscilloscope (DSO)

A digital oscilloscope (DSO) is a laboratory instrument used to display and analyse the waveform of electronic signals. We can use a DSO to measure various electrical signals, including voltage, current, frequency, and phase. *In our experiment, the DSO shows you the voltage plot as a function of time of an AC current.*

### Root Mean Square Voltage

In our experiment, an oscilloscope measures how voltage changes as time progresses. In other words, it detects the voltage as a function of time,  $V(t)$ . At home, you have many 3-pin sockets providing an AC voltage source. An AC voltage is typically varying like the sine curve; as time progresses,

$$V(t) = V_0 \sin(2\pi ft) \quad (1)$$

where  $V_0$  is the amplitude, and  $f$  is the frequency of the signal. You can imagine this as a fluctuating voltage battery that could automatically change its terminal signs (+ or -), too!

A sine signal pattern repeats as time progresses, and each pattern cycle takes about  $T$  seconds. Therefore, the frequency of

the signal is given by  $f = 1/T$  Hz. Suppose that you randomly pick  $N$  numbers between 0 sec and  $T$  secs, i.e.,  $t_1, t_2, t_3, \dots, t_N$ . With these, you can evaluate the corresponding values of voltages using Eq. (1), i.e.,

$$\begin{aligned} V_1 &= V_0 \sin(2\pi ft_1) \\ V_2 &= V_0 \sin(2\pi ft_2) \\ V_3 &= V_0 \sin(2\pi ft_3) \\ &\vdots \\ V_N &= V_0 \sin(2\pi ft_N) \end{aligned}$$

You can calculate the average using the standard formula,

$$\bar{V} = \frac{V_1 + V_2 + \dots + V_N}{N} \quad (2)$$

Voila! You have estimated the average of the voltage function,  $V(t)$ , over the period  $T$ . However, the sine signal fluctuates above and below 0V. So, the average voltage in Eq. (2) will be zero, which is not meaningful. To get a meaningful result, we are interested in the average of the magnitudes, regardless of the voltage sign. To make it easy, we just take the squares of each  $V(t_i)$ , because squaring a positive or negative number will always return a positive number! Therefore,

$$\overline{V^2} = \frac{V_1^2 + V_2^2 + V_3^2 \dots + V_N^2}{N} \quad (3)$$

However, Eq. (3) is the average of the squared of  $V_i$ . That is too large; therefore, engineers take the square root,

$$V_{rms} = \sqrt{\frac{V_1^2 + V_2^2 + V_3^2 \dots + V_N^2}{N}} \quad (4)$$

If you generate many, many, many random numbers  $t_i$ , i.e.,  $N \rightarrow \infty$ , then you have to use calculus,

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2 dt} \quad (5)$$

$$= \sqrt{\frac{1}{T} \int_0^T V_0^2 \sin^2(2\pi ft) dt}$$

$$V_{rms} = \frac{1}{\sqrt{2}} V_0$$

## EQUIPMENT

1. Battery (6 V)
2. Ammeter (0–30 mA)
3. Voltmeter (0–10 V)
4. Digital storage oscilloscope (DSO)
5. Audio frequency generator
6. Digital multimeter (DMM)
7. 10-decade potentiometers

## PROCEDURES

### Week 1 (Part A): Measuring resistance using Ammeters and Voltmeters

In this part of the experiment, you will use three different methods to measure the unknown resistance,  $R_x$ : (A1) using a voltmeter and an ammeter, (A2) using a graphical method by varying resistance and noting the current.

**Figure 5:** Circuit for the ammeter/voltmeter method.

#### A1: Ohms Law Method

1. Using a DMM, obtain the resistance value after subtracting the lead resistance. Take this as your true value of resistance.
2. Set up the circuit shown in **Figure 2** and obtain the resistance using Ohm's law,


$$R = \frac{V}{I} \quad (6)$$

3. We can estimate the error of  $R$  using the Propagation of Error formula,

$$\Delta R = R \sqrt{\left(\frac{\Delta V}{V}\right)^2 + \left(\frac{\Delta I}{I}\right)^2} \quad (7)$$

where  $\Delta R$ ,  $\Delta V$ , and  $\Delta I$  are the error of  $R$ , measured voltage, and measured current, respectively. Your final quote of  $R_x$  will be,

$$R_x = R \pm \Delta R \text{ Ohms}$$

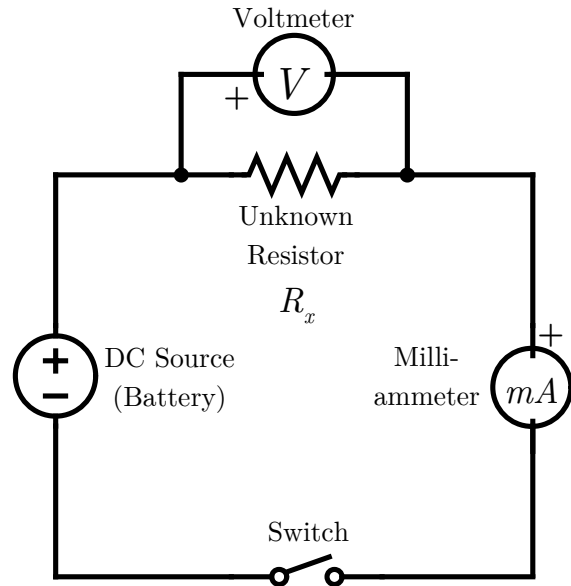

**Figure 2:** Circuit for the ammeter/voltmeter method.

#### A2: Empirical Method

In this part of the experiment, you will obtain the unknown resistance,  $R_x$ , using a plot of known resistance,  $R(I)$ , against the measured current.

1. Set the circuit as shown in **Figure 3**.
2. Set both  $R_0$  and  $R_1$  into  $0 \Omega$ .
3. Adjust  $R_0$  so that the milli-ammeter reading stays at 10 mA.
4. Notice that now  $R_1 = 0 \Omega$  due to Step 2. Record the milli-ammeter reading, and this corresponds to  $I(0)$ .
5. Now, repeat Step 4, but adjust  $R_1$  into other values and record corresponding ammeter readings for  $R_1 = 100\Omega, 200\Omega, \dots, 1000\Omega$ .

6. Prepare a table like in Table 1. For each row, calculate  $a_i$ ,

$$a_i = -\frac{1}{R_i} \ln \left( \frac{I_i}{10} \right) \quad (8)$$

Table 1

$R_1 (\Omega)$	$I_i$ (mA)	$a_i$
0	10.0	–
100	$I_1 \pm \Delta I$	$a_1$
200	$I_2 \pm \Delta I$	$a_2$
$\vdots$	$\vdots$	$\vdots$
1000	$I_{10} \pm \Delta I$	$a_{10}$

7. Make a plot of current vs. resistance recorded in the above table. Obtain

$$\alpha = \frac{a_1 + a_2 + \cdots + a_{10}}{10} \quad (9)$$

8. Replace  $R_1$  with  $R_x$ . Obtain the milli-ammeter reading,  $I_x$ . Obtain  $R_x$  using Eq. (3),

$$I_x = 10e^{-\alpha R_x} \quad (10)$$

where  $\alpha$  is the value that you have obtained in Step 7.

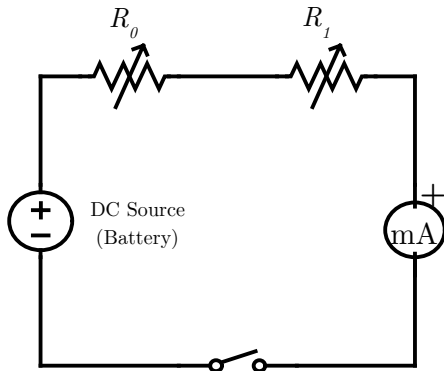



Figure 3: Circuit for the graphical method.

## Part B: Using an Oscilloscope

In this part, you will use the DSO to measure (a) measure the amplitude and frequency of an AC Voltage and (b) verify that,  $V_{\text{rms}} = \frac{1}{\sqrt{2}} V_0$ , where  $V_{\text{rms}}$  is the root mean square voltage, and  $V_0$  is the amplitude of the AC voltage.

### Setting up the AC Source


1. Turn on the AC source power.
2. Toggle the attenuation knob to 0 dB.
3. Adjust the output level knob to the middle position.
4. Adjust the frequency level knob to any value. You can use the dial on the AC source as a guide.

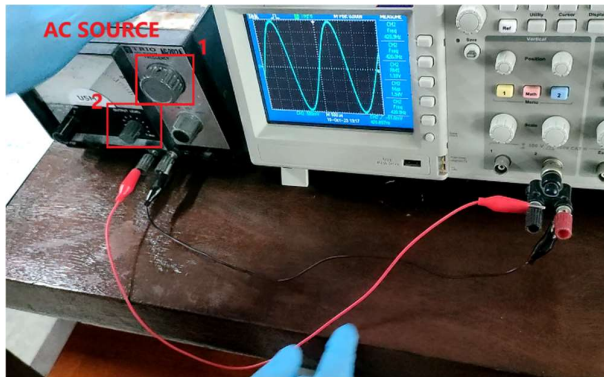

**Figure 4:** The connection for Part B. (1) The frequency level knob. (2) The output level knob.

### Setting up the Oscilloscope.

1. Set up the circuit connection as in Figure 1. You don't have to worry about polarity (+ or – signs).
2. Turn on the oscilloscope and press the *Autoset* button (Figure 5). Please wait for it to set up.
3. If the display is frustrating, adjust the output level knob and repeat step 2.

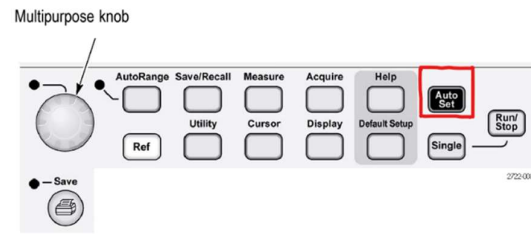


**Figure 5:** The Autoset button.

### Verifying the relationship between root mean square voltage, $V_{\text{rms}}$ and amplitude, $V_0$ .

In this part, you will plot the peak voltage versus the RMS voltage of the sine wave. Refer to Figure 6.

1. Push the *Measure* button (1) to see the Measure Menu.
2. Push the topmost option button (2); then the Measure 1 menu appears.
3. Push *Source* ► CH2 (depends on which terminal you connect the AC source).
4. Push *Type* ► Max.
5. Push the *Back* option button.
6. Push the second option button (3) from the top; the Measure 2 Menu appears.
7. Push *Source* ► CH2 (depends on which terminal you connect the AC source).
8. Push *Type* ► Cyc RMS.
9. Push the *Back* option button.
10. From the oscilloscope screen (next to each corresponding option button), obtain the  $V_{\text{max}}$  and the corresponding  $V_{\text{rms}}$ .
11. Repeat this for the various  $V_{\text{max}}$  values (adjust using the *output level* knob of the AC source) and record the ( $V_{\text{max}}$ ,  $V_{\text{rms}}$ ) pair in Table 2 of your worksheet (Part B).
12. Follow the remaining instructions in the worksheet.

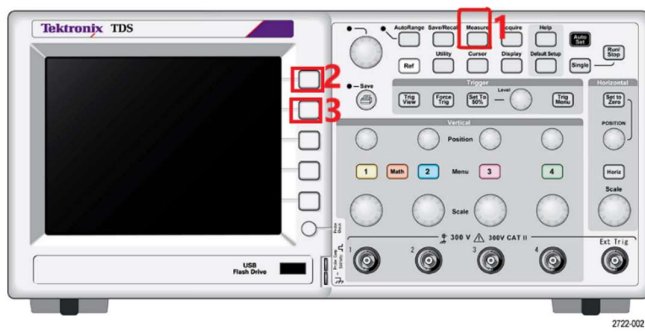

**Figure 6:** Oscilloscope buttons. (1) The measure button. (2) First option button, topmost. (3) Second option button.

*Last Updated: 23 March 2024 (MRO)*

# BASIC ELECTRICAL MEASUREMENTS WORKSHEET

*Instructions:* Please **submit this worksheet at the end of the second session** of your experiment.

Name : \_\_\_\_\_  
 Group : \_\_\_\_\_  
 Partner's : \_\_\_\_\_  
 Name : \_\_\_\_\_  
 Marks : \_\_\_\_\_

## DATA

### Part A1: Ammeter / Voltmeter Method

1. The true value of resistance (measured using a digital multimeter (DMM):

First measurement ( $R_1$ ):

---

  $\Omega$ 

Second measurement ( $R_2$ ):

---

  $\Omega$ 

Third measurement ( $R_3$ )t:

---

  $\Omega$ 

Average:

---

2. Value of resistance using Ohm's Law  
(show your workings below):

a) Current ( $I$ ):

\_\_\_\_\_ ± \_\_\_\_\_

b) Voltage ( $V$ ):

\_\_\_\_\_ ± \_\_\_\_\_

c) Resistance ( $R$ ) using Eqs. (6) & (7):

\_\_\_\_\_ ± \_\_\_\_\_

## Part A2: Empirical Method

Table 1: Resistance versus current.

Resistance, $R$ ( $\Omega$ )	Current, $I$ (mA)	$a_i$
0	$\pm$	-
100	$\pm$	
200	$\pm$	
300	$\pm$	
400	$\pm$	
500	$\pm$	
600	$\pm$	
700	$\pm$	
800	$\pm$	
900	$\pm$	
1000	$\pm$	
	Average of $a_i$ ( $\alpha$ )	
$R_x$	$\pm$	

From Eq. (10), the value of  $R_x$  is given by \_\_\_\_\_  $\Omega$ .

Calculate the percentage discrepancy between the measurement made using (1) the digital multimeter (DMM) and (2) the multimeter with the value of resistance obtained through the colour code:

## DISCUSSION & CONCLUSION

### (PART A)

*Safety Precautions:*

[illegible]

*Comments about your findings:*

*Potential Sources of Error:*

*Conclusions:*

-----The End of Part A (Week 1)-----

## Part B2: Measurement of AC Voltage

**Table 2:** Peak voltage versus the RMS voltage.

Peak Voltage ( $V_p$ )	RMS Voltage ( $V_{RMS}$ )	$m = \frac{V_{RMS}}{V_0}$
Average of $m$ :		

From the above result (average of  $m$ ), obtain the slope of the straight line and compare this value with the theoretical value,  $\frac{1}{\sqrt{2}}$ . Calculate its percentage discrepancy.

## DISCUSSION AND CONCLUSION (PART B)

*Safety Precautions:*

[illegible]

### Potential Sources of Error.

[illegible]



[illegible]

Comments about your findings:

[illegible]

---

---

---

*Conclusions:*

[illegible]

-----The End of Part B (Week 2)-----